
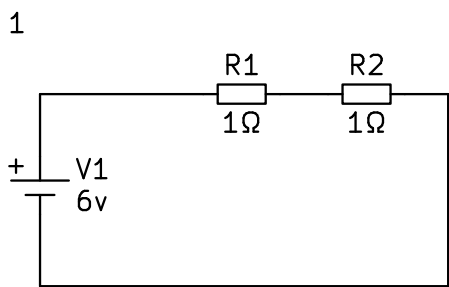


RESISTENCIAS EQUIVALENTES EN SERIE Y PARALELO LÁMINA 1


ALUMNO: _____ GRUPO: _____ FECHA: _____

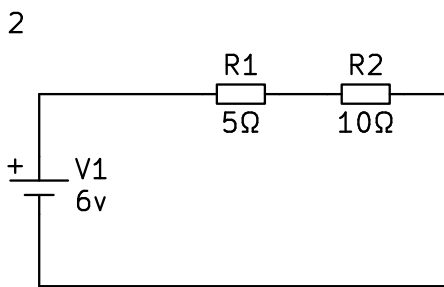


$R_{total} =$
 $I =$




$R_{total} =$
 $I =$

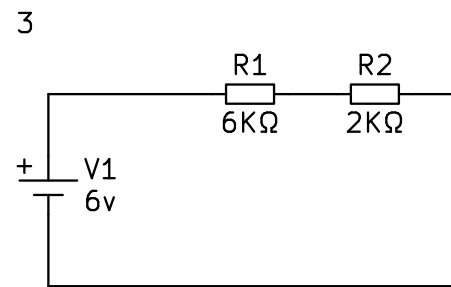


$R_{total} =$
 $I =$

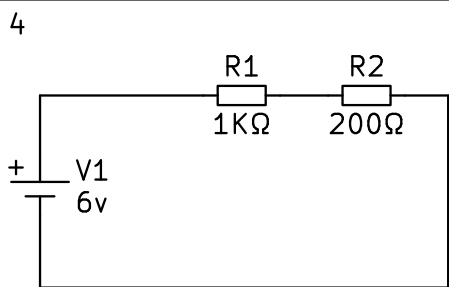


$R_{total} =$
 $I =$

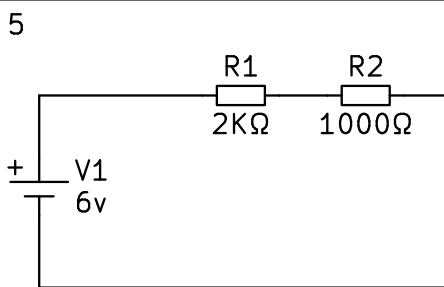


$R_{total} =$
 $I =$

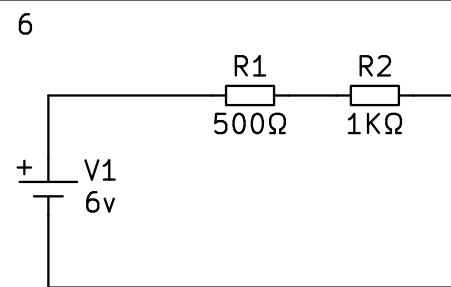


$R_{total} =$
 $I =$

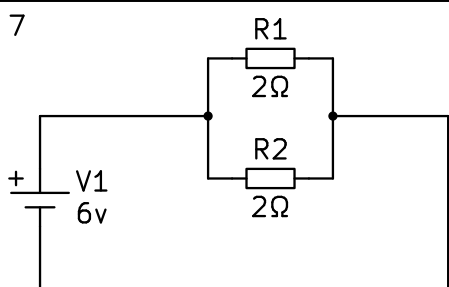


$R_{total} =$
 $I =$

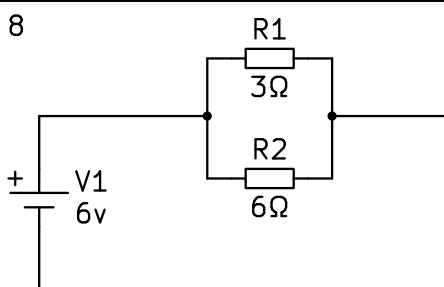


$R_{total} =$
 $I =$

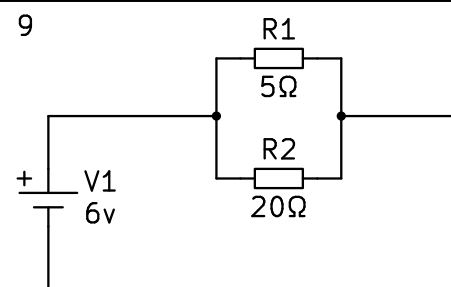


$R_{total} =$
 $I =$

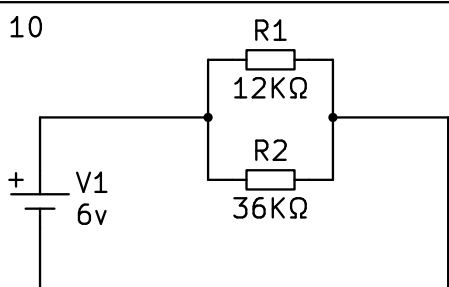


$R_{total} =$
 $I =$

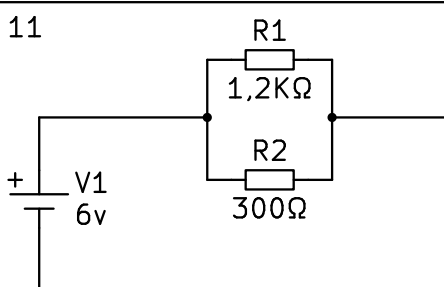


$R_{total} =$
 $I =$

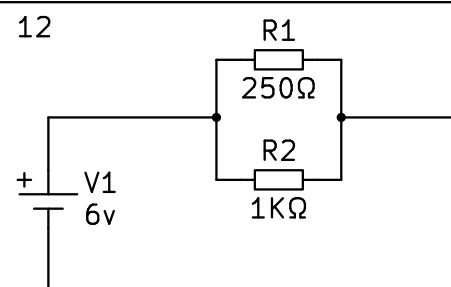


$R_{total} =$
 $I =$

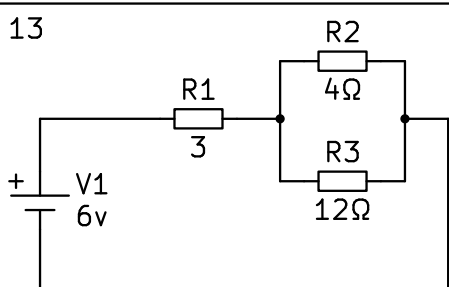

$R_{total} =$
 $I =$

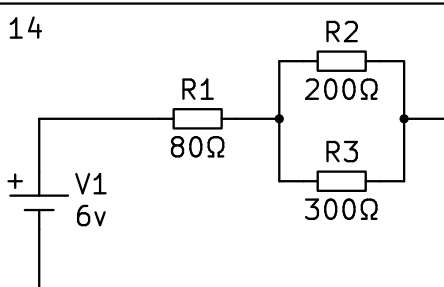


$R_{total} =$
 $I =$

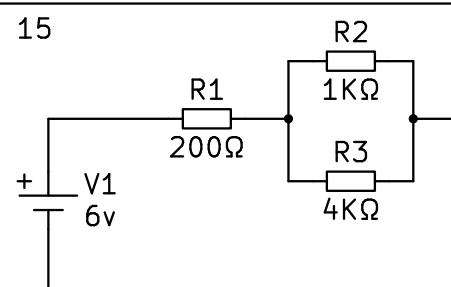


$R_{total} =$
 $I =$

ALUMNO: _____ GRUPO: _____ FECHA: _____

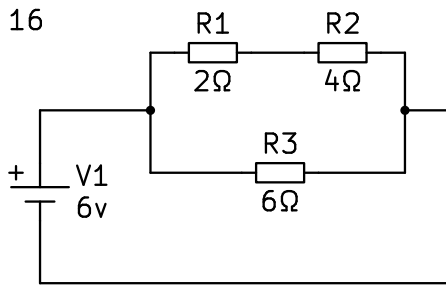


$R_{total} =$

$I =$

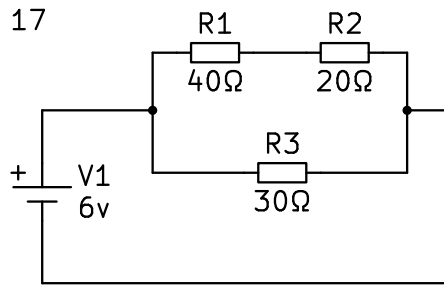


$R_{total} =$

$I =$

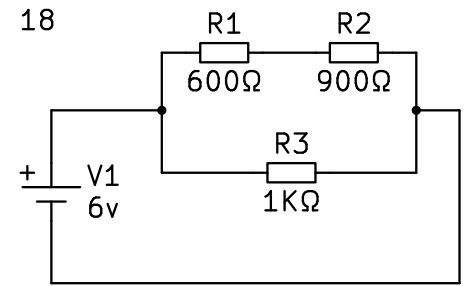


$R_{total} =$

$I =$

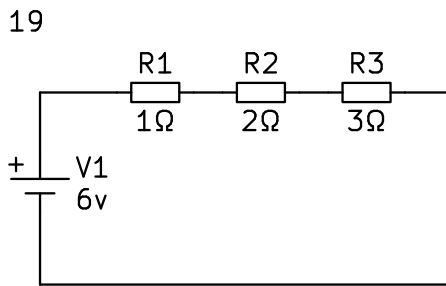


$R_{total} =$

$I =$

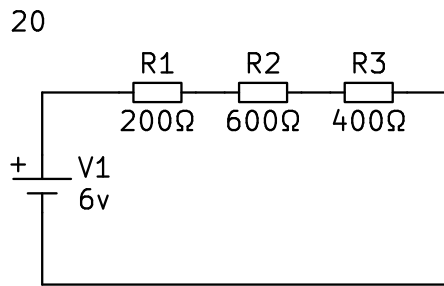


$R_{total} =$

$I =$

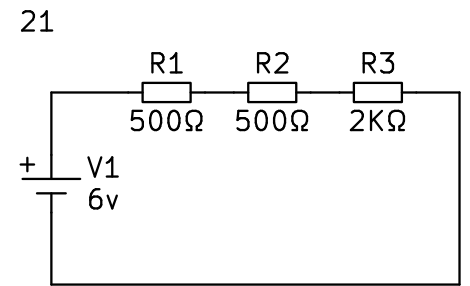


$R_{total} =$

$I =$

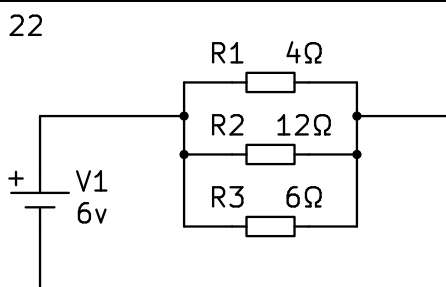


$R_{total} =$

$I =$

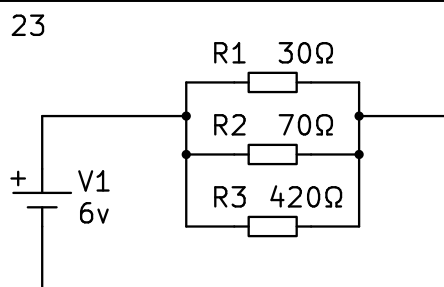


$R_{total} =$

$I =$

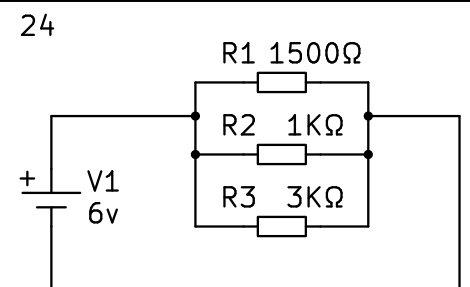


$R_{total} =$

$I =$

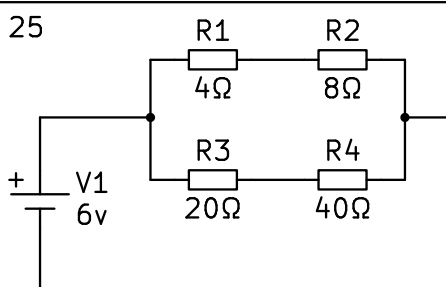


$R_{total} =$

$I =$

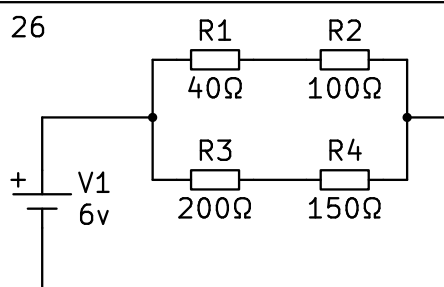


$R_{total} =$

$I =$

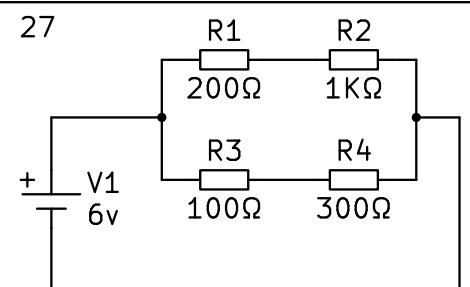


$R_{total} =$

$I =$

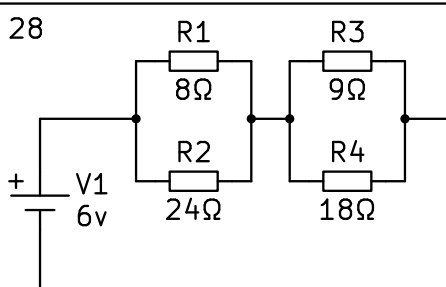


$R_{total} =$

$I =$

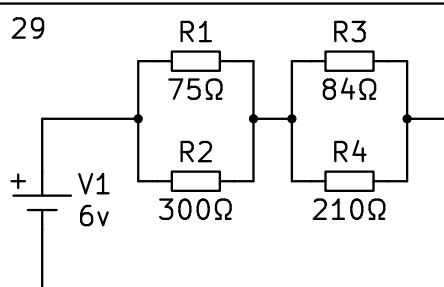

$R_{total} =$

$I =$

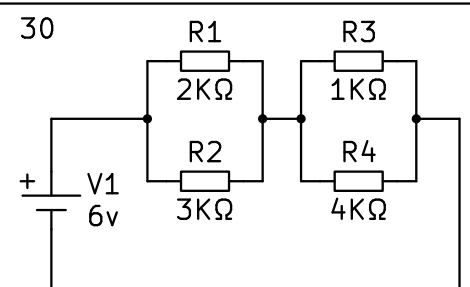

$R_{total} =$

$I =$